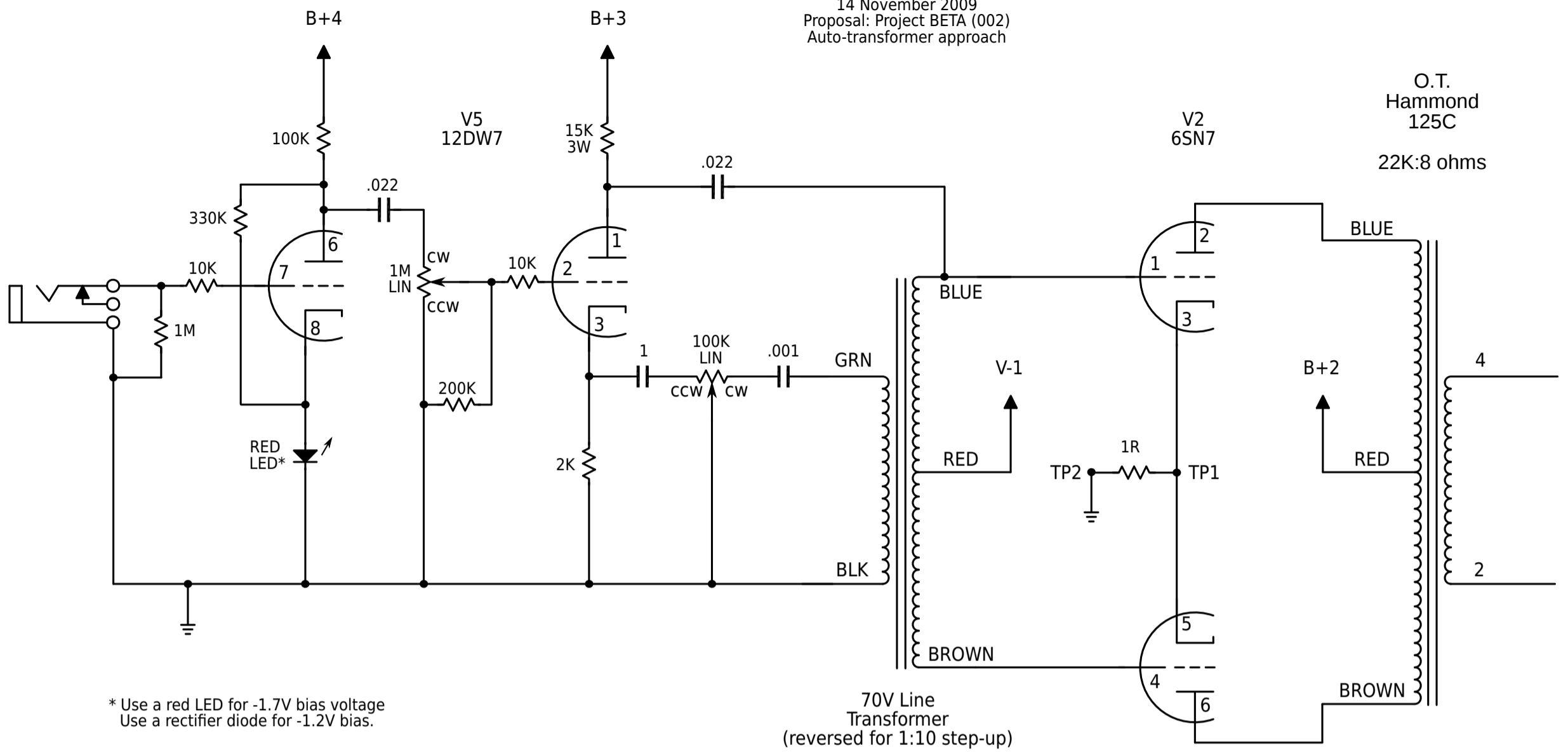


Stephen Keller
 14 November 2009
 Proposal: Project BETA (002)
 Auto-transformer approach



* Use a red LED for -1.7V bias voltage
 Use a rectifier diode for -1.2V bias.

